

ARITHMETIC HARDWARE

Introduction


- Adders
 - Half
 - Full
 - Ripple-Carry
 - Carry-Lookahead
 - Carry-Select
- Arithmetic Logic Unit

1-Bit Half Adder

A	B	Sum	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


- $\text{Sum} = A'B + AB'$
- $\text{Cout} = AB$

1-Bit Half Adder

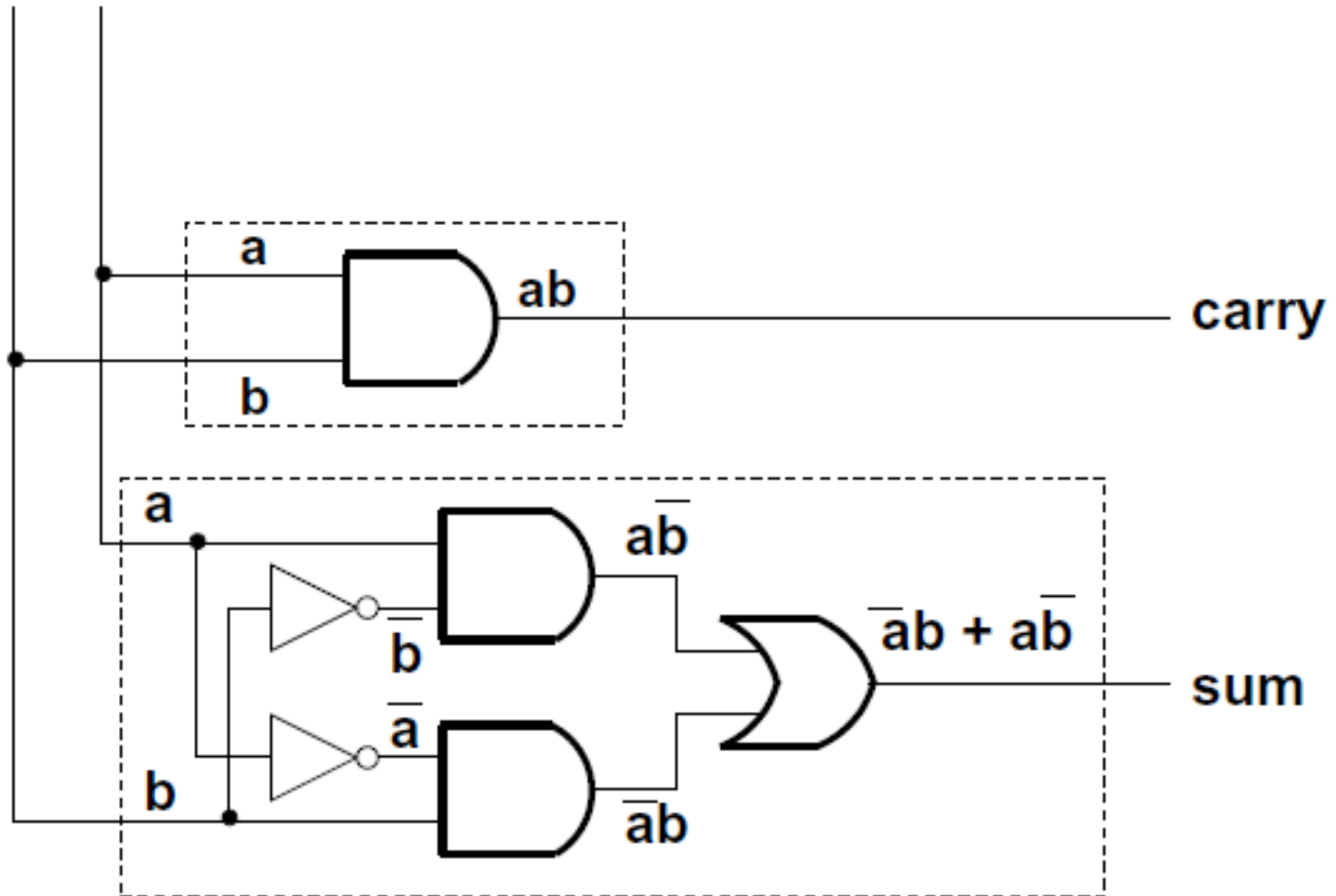


1-Bit Half Adder

- Sum = $A'B + AB'$
= A XOR B

 

1-Bit Half Adder

- Block Diagram

 


1-Bit Full Adder

- $\text{Sum} = A \text{ XOR } B \text{ XOR } \text{Cin}$
- $\text{Cout} = AB + AC_{\text{in}} + BC_{\text{in}}$

Inputs			Outputs		Comments
A	B	Cin	Cout	Sum	
0	0	0	0	0	$0+0+0=00$
0	0	1	0	1	$0+0+1=01$
0	1	0	0	1	$0+1+0=01$
0	1	1	1	0	$0+1+1=10$
1	0	0	0	1	$1+0+0=01$
1	0	1	1	0	$1+0+1=10$
1	1	0	1	0	$1+1+0=10$
1	1	1	1	1	$1+1+1=11$


1-Bit Full Adder

 - Standard approach
 - 6 gates
 - 2 XORs, 2 ANDs, 2 ORs




1-Bit Full Adder

 - Alternative implementation
 - 5 gates
 - half adder is an XOR gate and AND gate
 - 2 XORs, 2 ANDs, 1 OR




1-Bit Full Adder

 


Ripple-Carry Adder

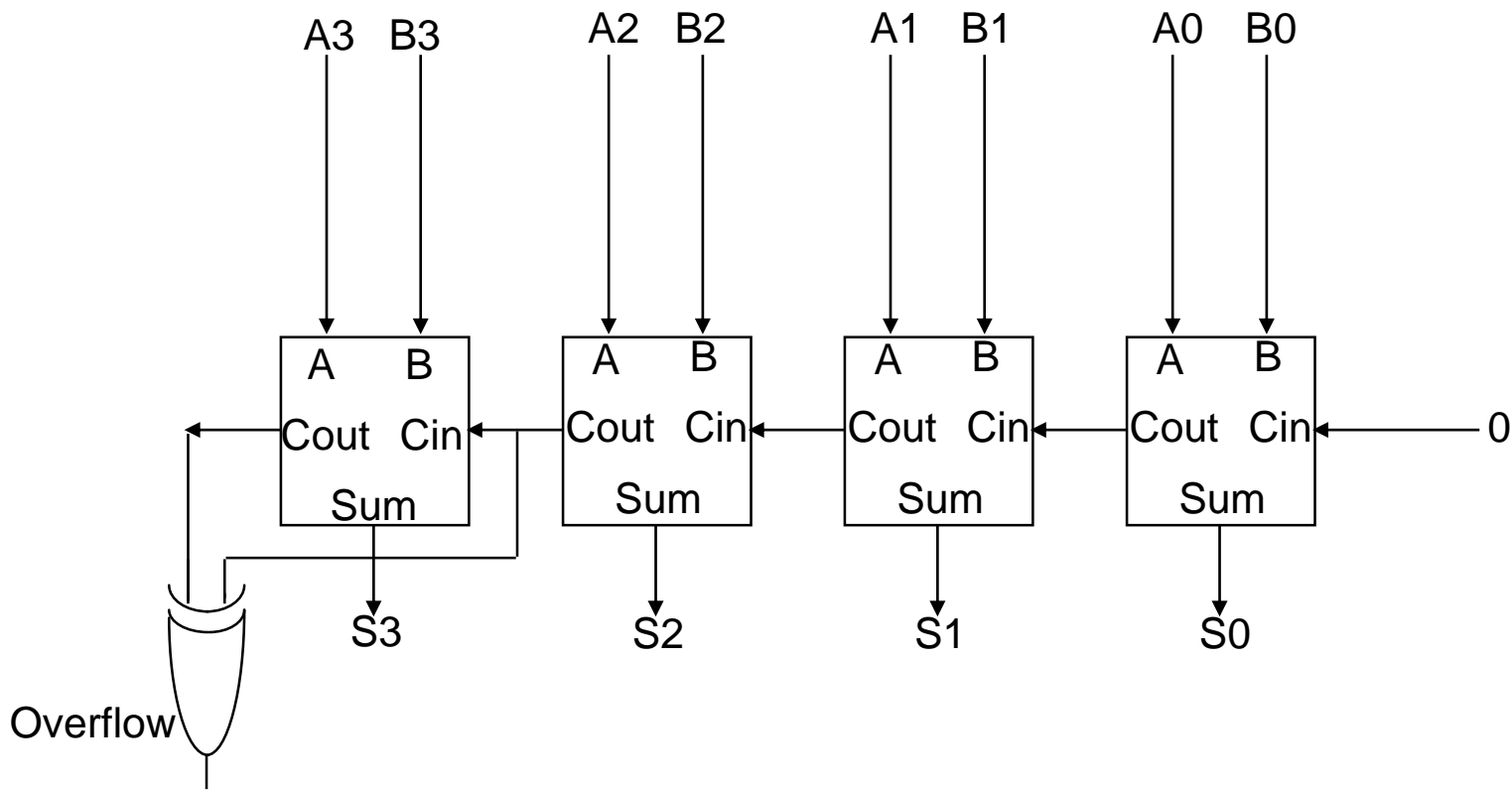- To add binary numbers of lengths greater than 1, we cascade one bit adders together.




Ripple-Carry Adder: Example

- $3 + 2 = 5$
- $0011 + 0010 = 0101$

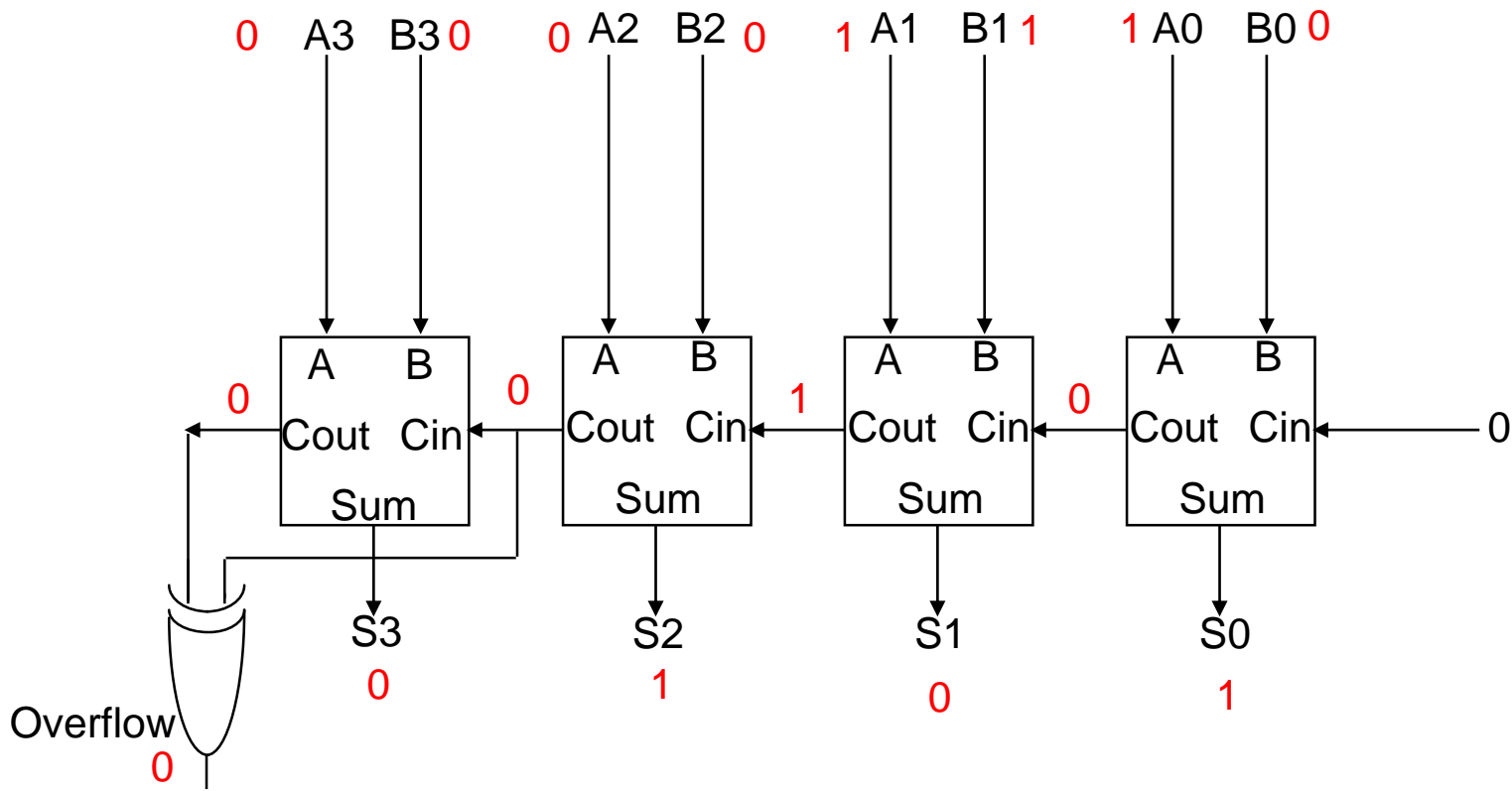


Ripple-Carry Adder: Subtraction

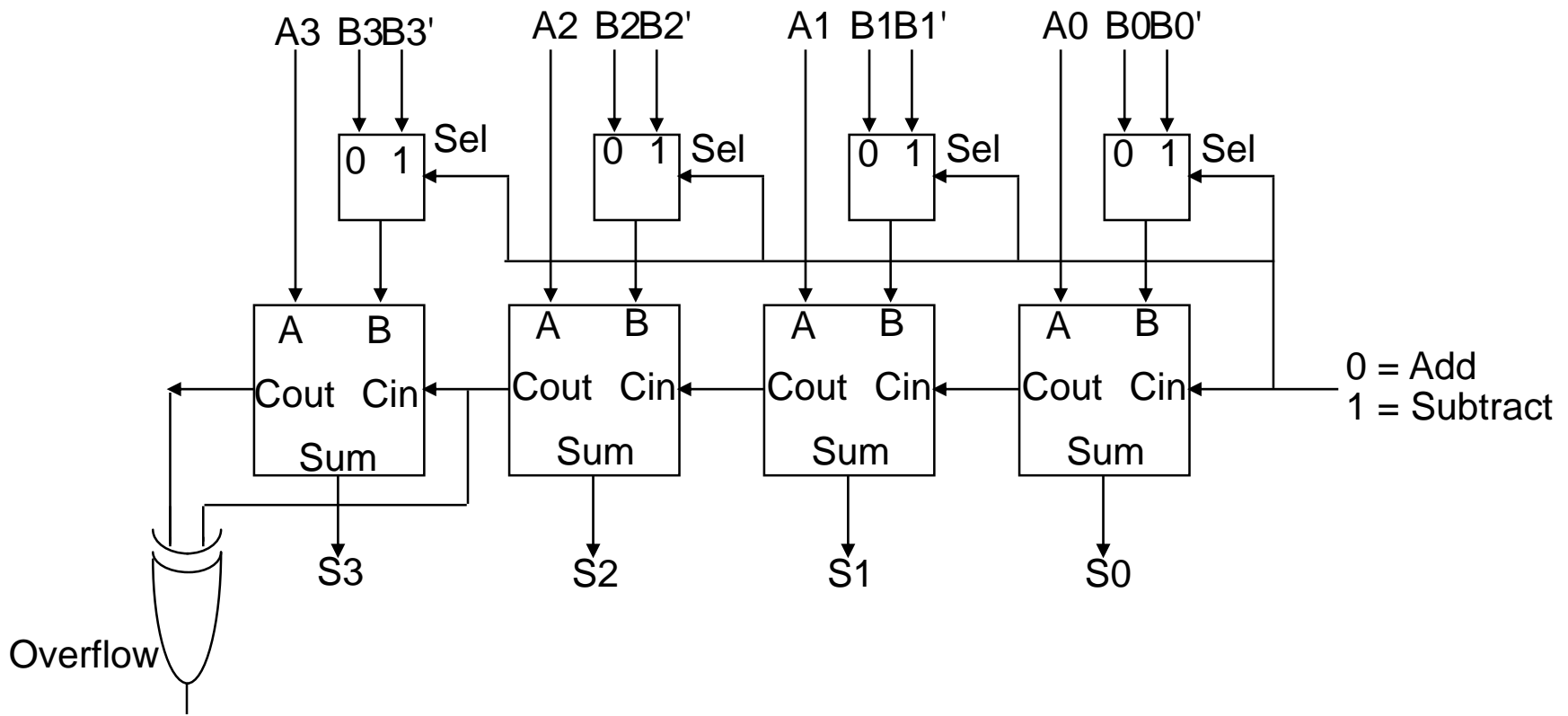- Use adders to subtract with 2s complement representation
 - $A - B = A + (-B) = A + B' + 1$





Ripple-Carry Adder: Subtraction

- $7 - 6 = 1$
- $0111 - 0110 = 0001$

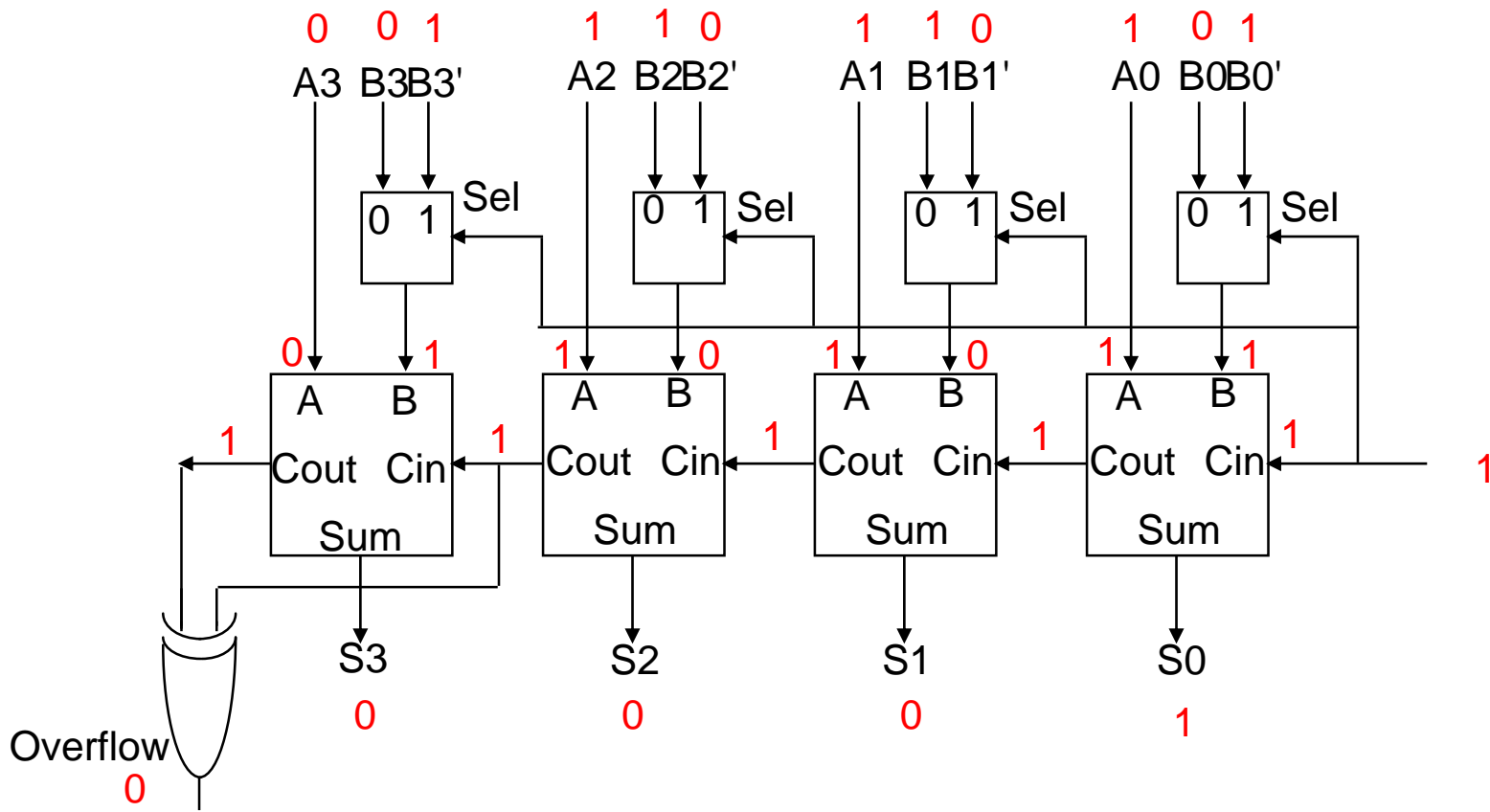

Ripple-Carry Adder: Disadvantage

 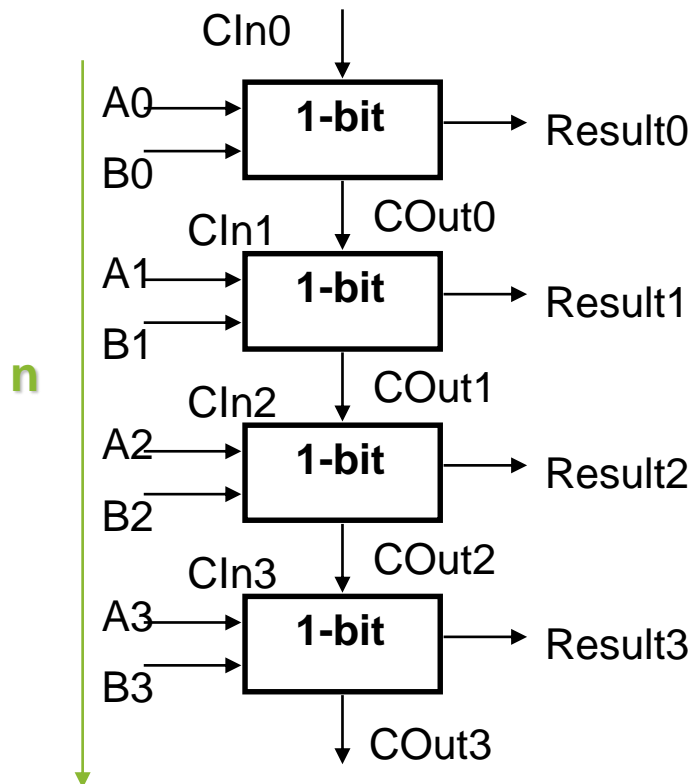- Long Delay
 - Carry bit may have to propagate from LSB to MSB
 - Worst case delay for n-bit adder = $2n$ gate delays



Ripple-Carry Adder

- Long delay due to the propagation of carry from low to high order stages
- The key to speeding up addition is determining carry values sooner.

Carry-Lookahead

- Determine the CarryOut:
 - $C_{out} = AB + AC_{in} + BC_{in} = AB + C_{in}(A+B)$

A	B	Cout	Comment
0	0	0	Carry terminate
0	1	Cin	Carry propagate
1	0	Cin	Carry propagate
1	1	1	Carry generate

Carry-Lookahead Logic


- Carry generate: $G_i = A_i B_i$
 - Must generate carry when $A = B = 1$
- Carry propagate: $P_i = A_i + B_i$
 - Carry-in will equal carry-out here
- Cout can be re-expressed these terms:
 - $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$
 $= A_i B_i + C_i (A_i + B_i)$
 $= G_i + C_i P_i$

Carry-Lookahead Logic




- Assume we have a 4-bit adder:
 - $C_1 = G_0 + P_0 C_0$
 - $C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$
 - $C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
 - $C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Each of the carry equations can be implemented with two-level logic
 - All inputs are now directly derived from data inputs and not from intermediate carries
 - this allows computation of all sum outputs to proceed in parallel

Carry-Lookahead Implementation

 - Adder with propagate and generate outputs




increasingly complex
logic for carries

   


Partial Carry Lookahead Adder

 - Very expensive to build “full” carry lookahead adder
 - Imagine the length of the equation for C_{in31} !
- In practice:
 - Connect several N-bit lookahead adders
 - Example: four 8-bit carry lookahead adders can form a 32-bit partial carry lookahead adder



Carry-Select Adder

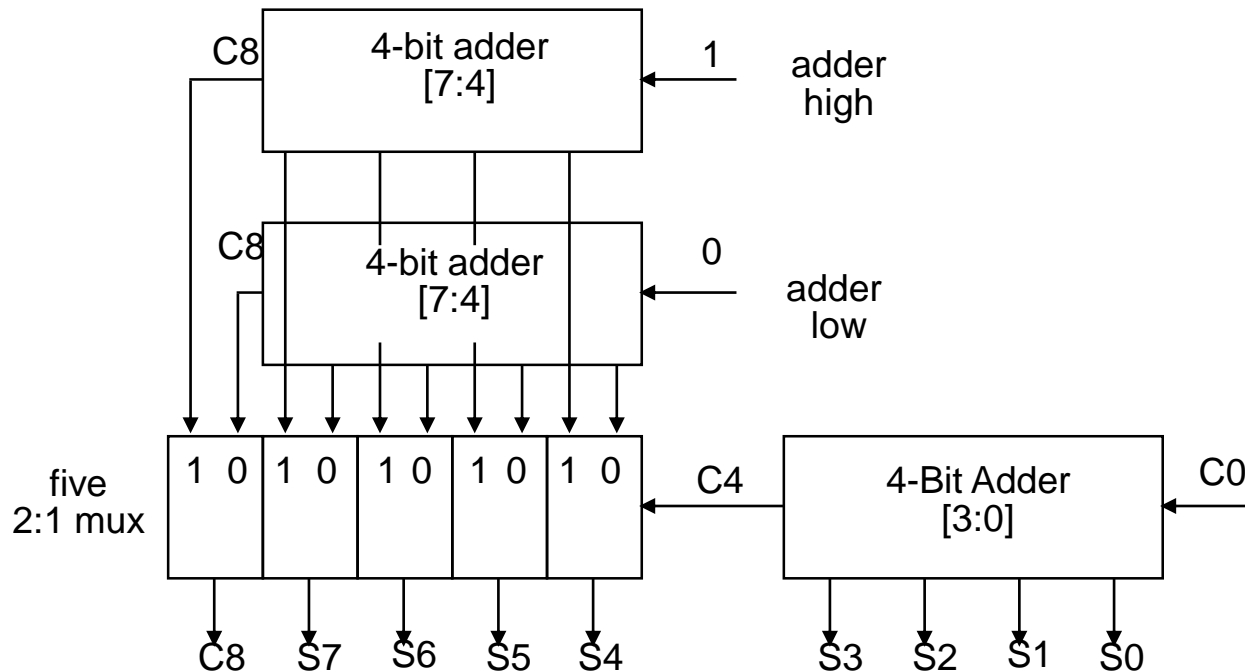- Redundant hardware to make carry calculation go faster
 - Compute two high-order sums in parallel while waiting for carry-in
 - One assuming carry-in is 0 and another assuming carry-in is 1
 - Select correct result once carry-in is finally computed



Arithmetic Logic Unit


- The Arithmetic Logic Unit (ALU) is the brawn of the computer
 - Performs arithmetic operations (addition, subtraction)
 - Performs logical operations (AND, OR, NOR)
 - Performs logical comparisons (Less Than, Equal To)

Arithmetic Logic Unit

- We will need (at least) a 32-bit ALU
 - Connect 32 1-bit ALUs together

AND, OR

- Uses: AND gate, OR gate, 2:1 mux

 


Addition

- Add a 1-bit full adder

Addition

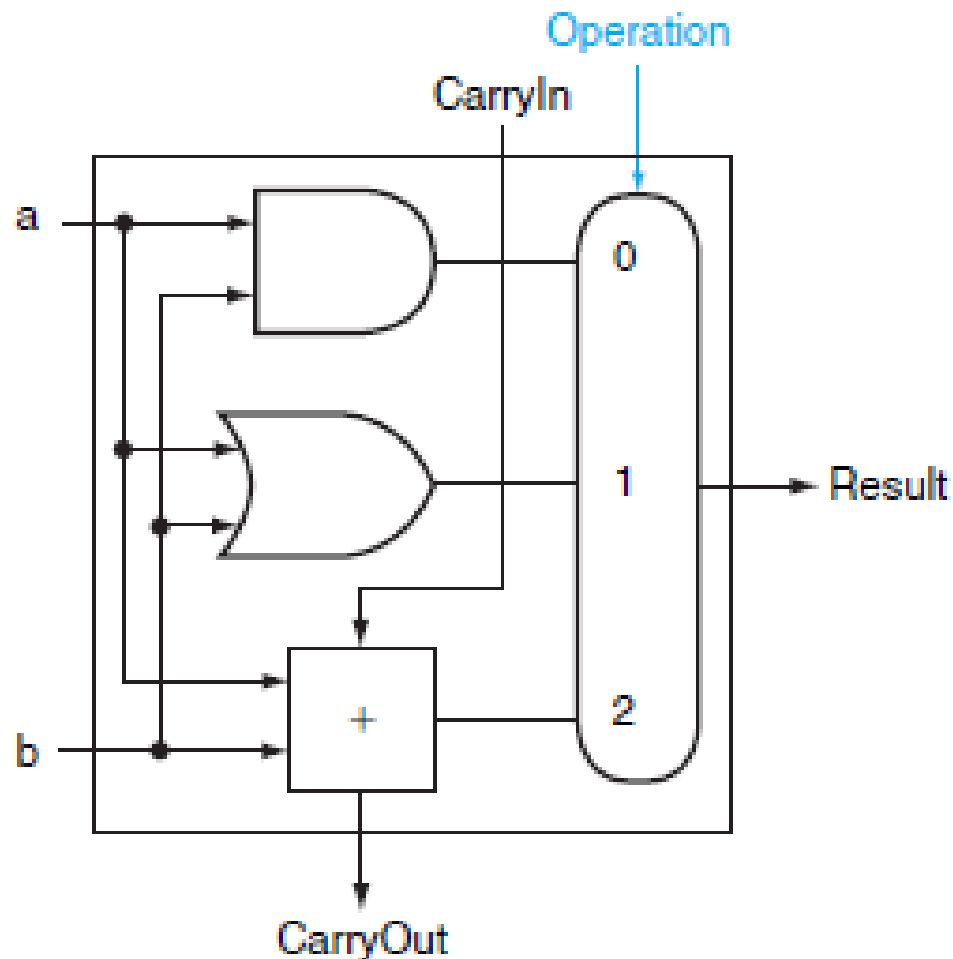
- This 1-bit ALU will perform AND, OR, and ADD



Subtraction

- $(A - B)$ is equivalent to $A + (-B)$
 - Take 2's complement of B and add A
 - 2's Complement: invert every bit and add 1
- To invert B
 - Add a 2:1 mux that chooses between b and b'
- To add 1
 - Set the CarryIn to 1 instead of 0


Subtraction

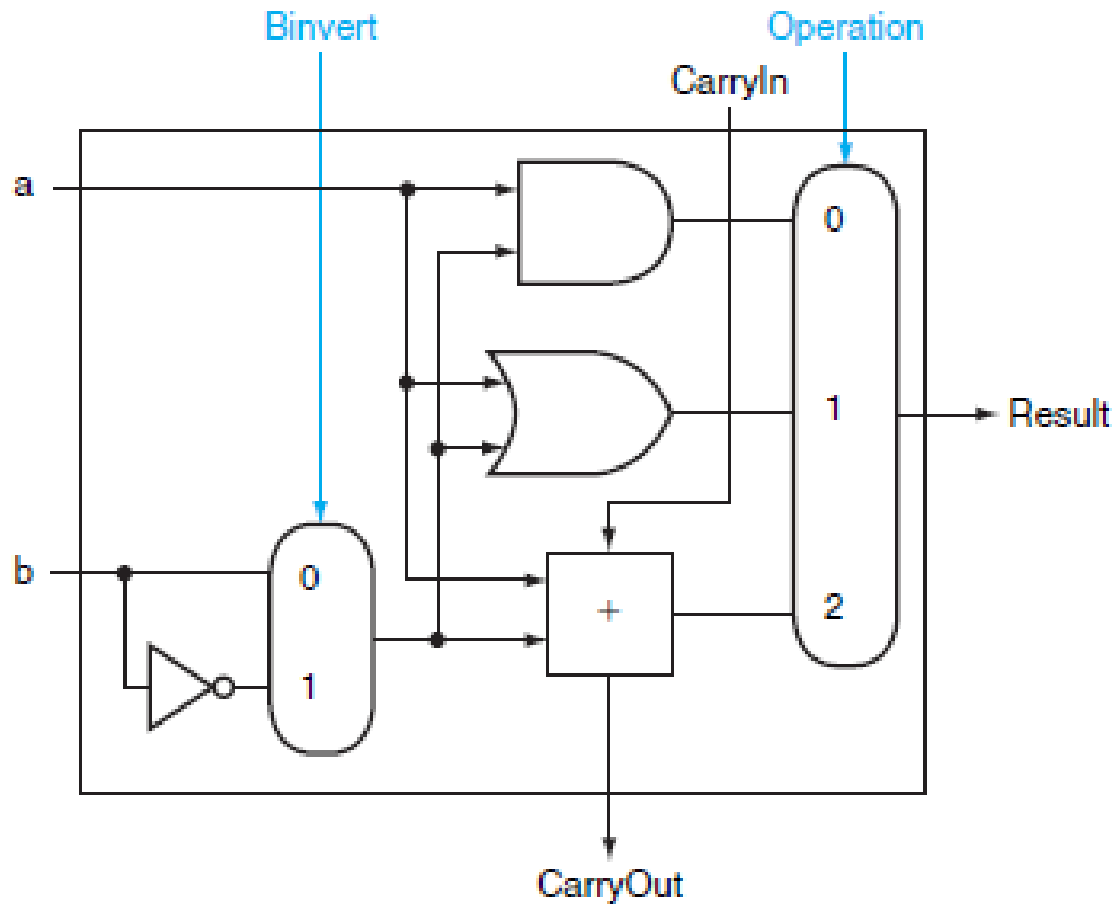

NOR

- $\text{NOR} = \text{NOT} (A \text{ OR } B)$
 $= (A + B)'$
 $= A' * B'$
 $= A' \text{ AND } B'$
- We already have an AND gate and an inverter for B
 - Add an inverter for A

NOR

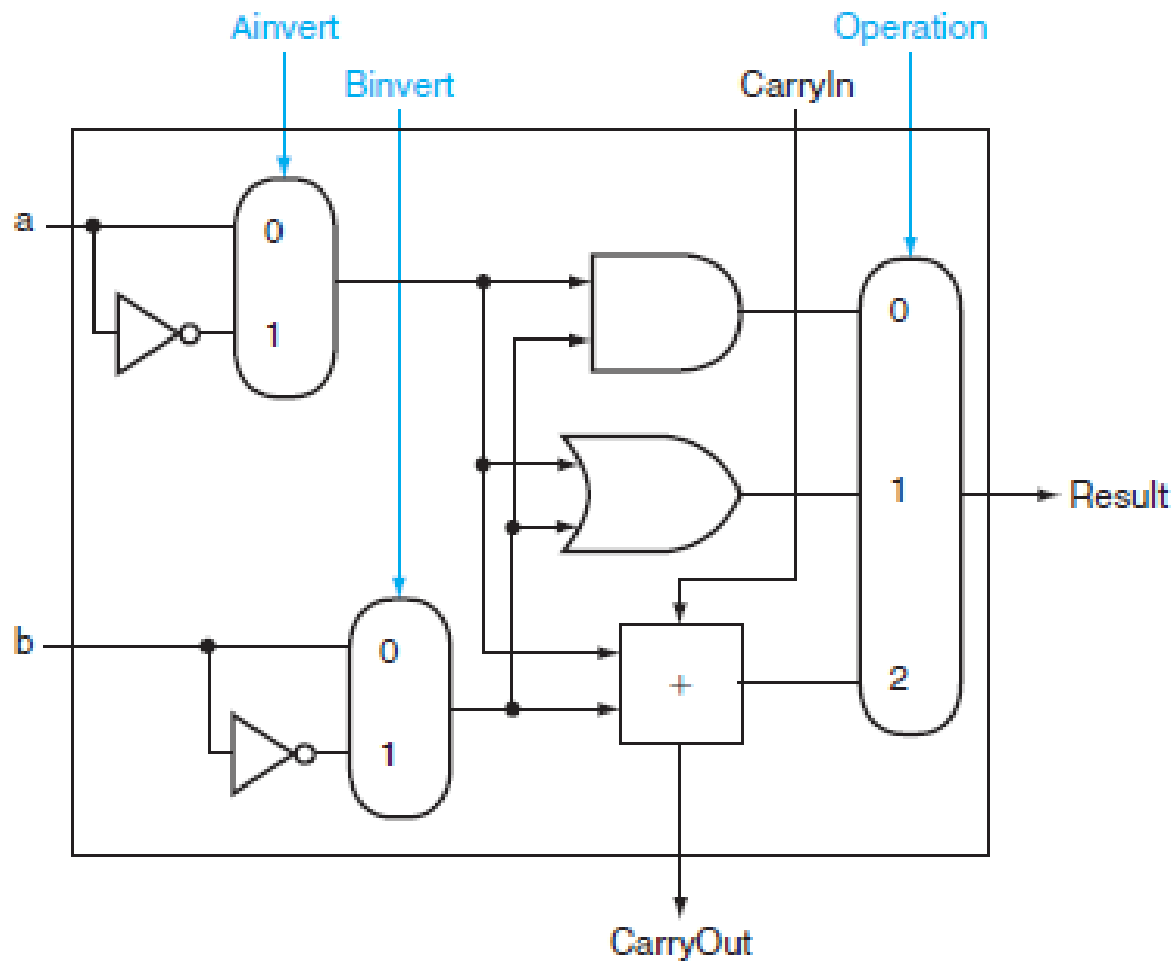

Set on Less Than

- Set on Less Than (slt) is a MIPS instruction
- For inputs A and B it produces 1 if $A < B$, 0 otherwise
- All bits are set to zero except for the least significant
 - Least significant bit determined by the result of $A < B$

Set on Less Than



- For our ALU to perform this operation we need:
 - A bigger mux
 - Input for the slt (called Less)
 - Method for determining if $A < B$

Set on Less Than

- $A < B$
- $A - B < 0$
 - Subtract and check the sign of the result
 - 1 if less than 0
 - 0 otherwise


Set on Less Than

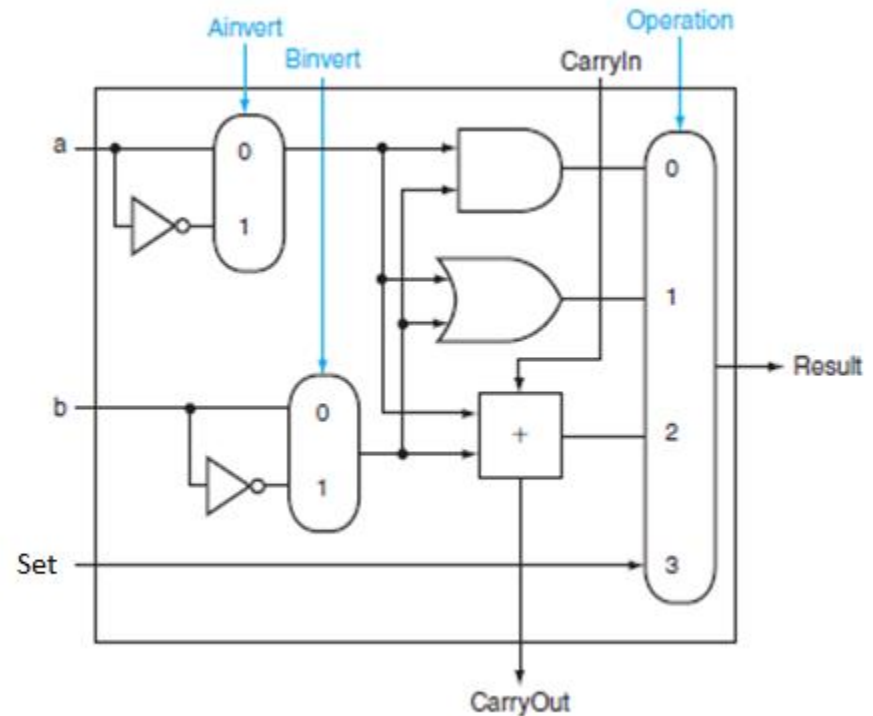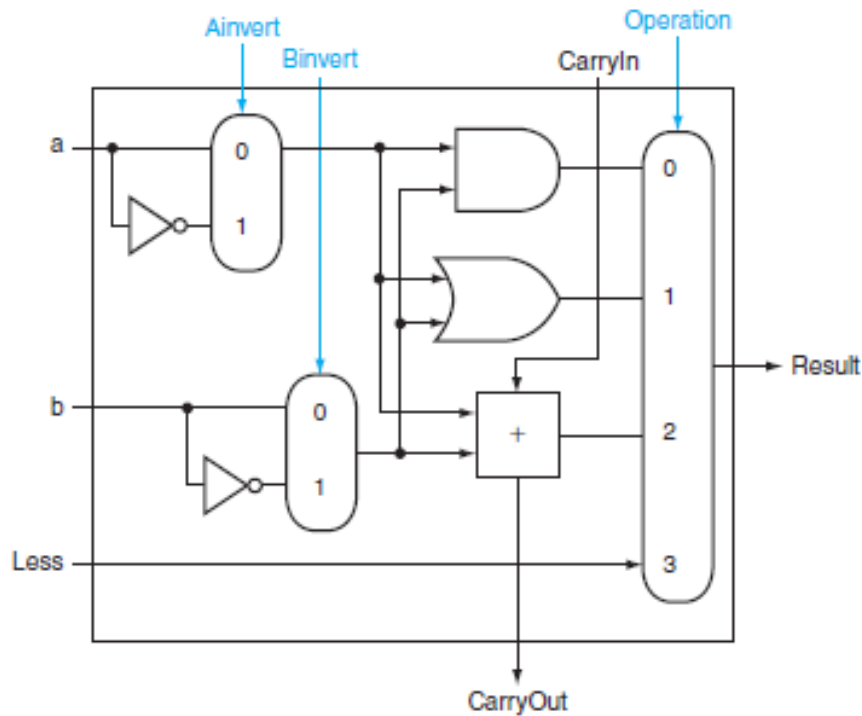- Bits 1-31: Less = 0
- Bit 0: sign bit of A-B



Set on Less Than

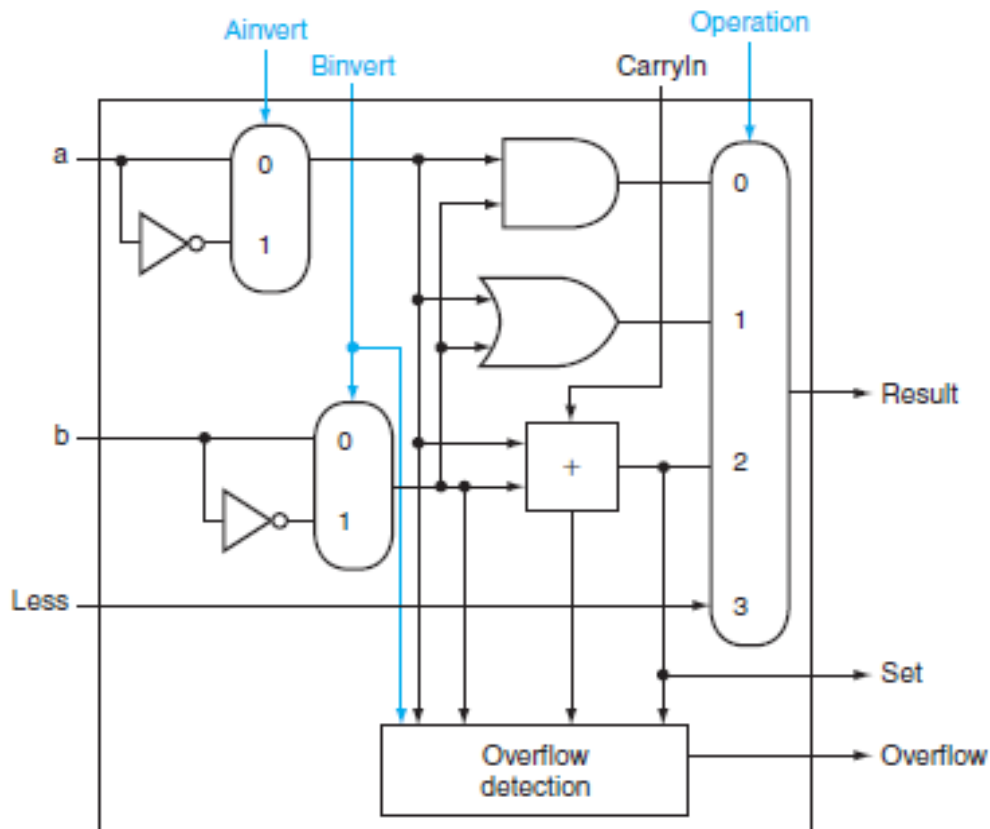- “Set” generate by most significant bit:




Equal To

- $A = B$
- $A - B = 0$
 - Subtract and check to see if all bits are zero
 - NOR all bits

Equal To

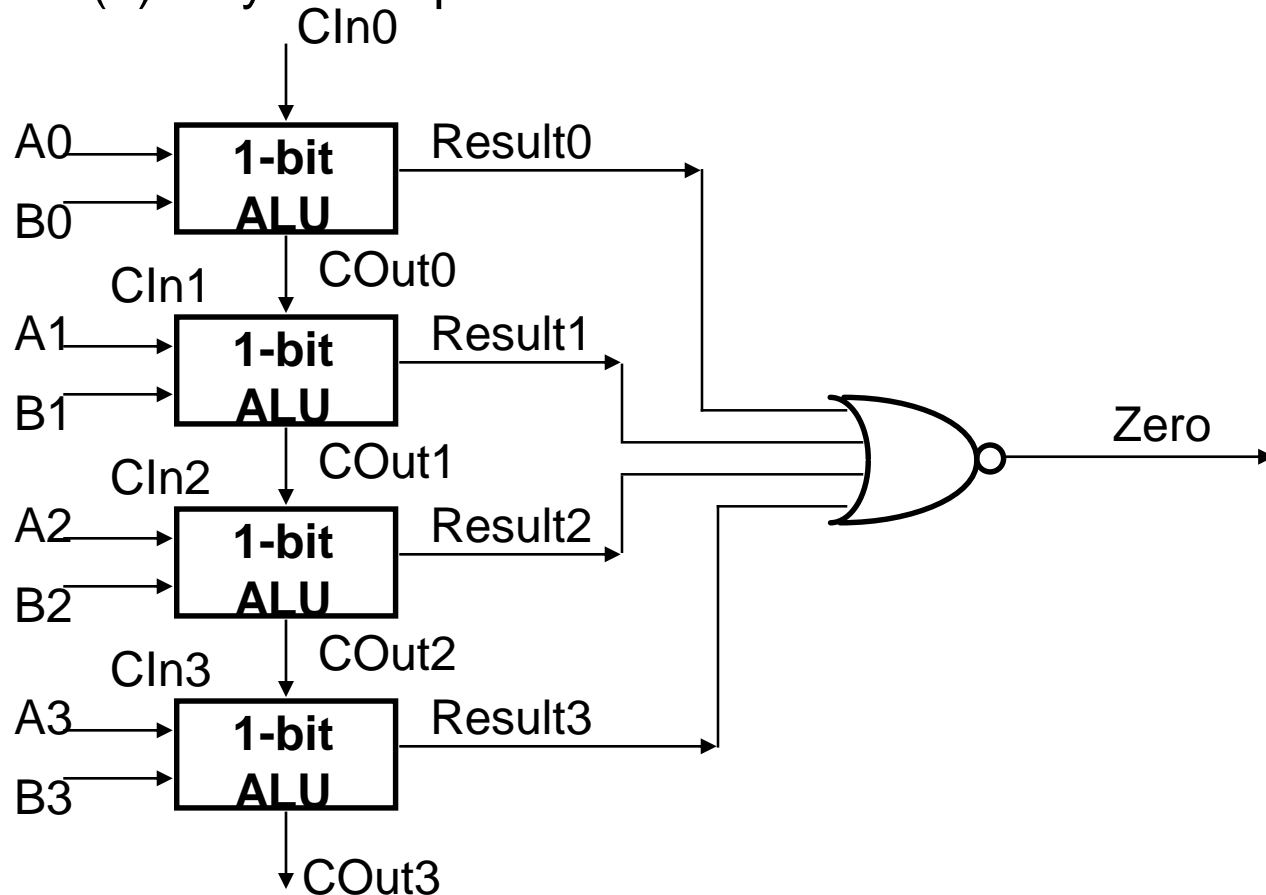
- Zero Detection Logic is just a NOR gate
 - Output true (1) only if *all* inputs zero



A 32-Bit ALU


- **Connect:**

 - 31 ALUs without overflow detection
- 1 ALU with overflow detection (MSB)



A 32-Bit ALU

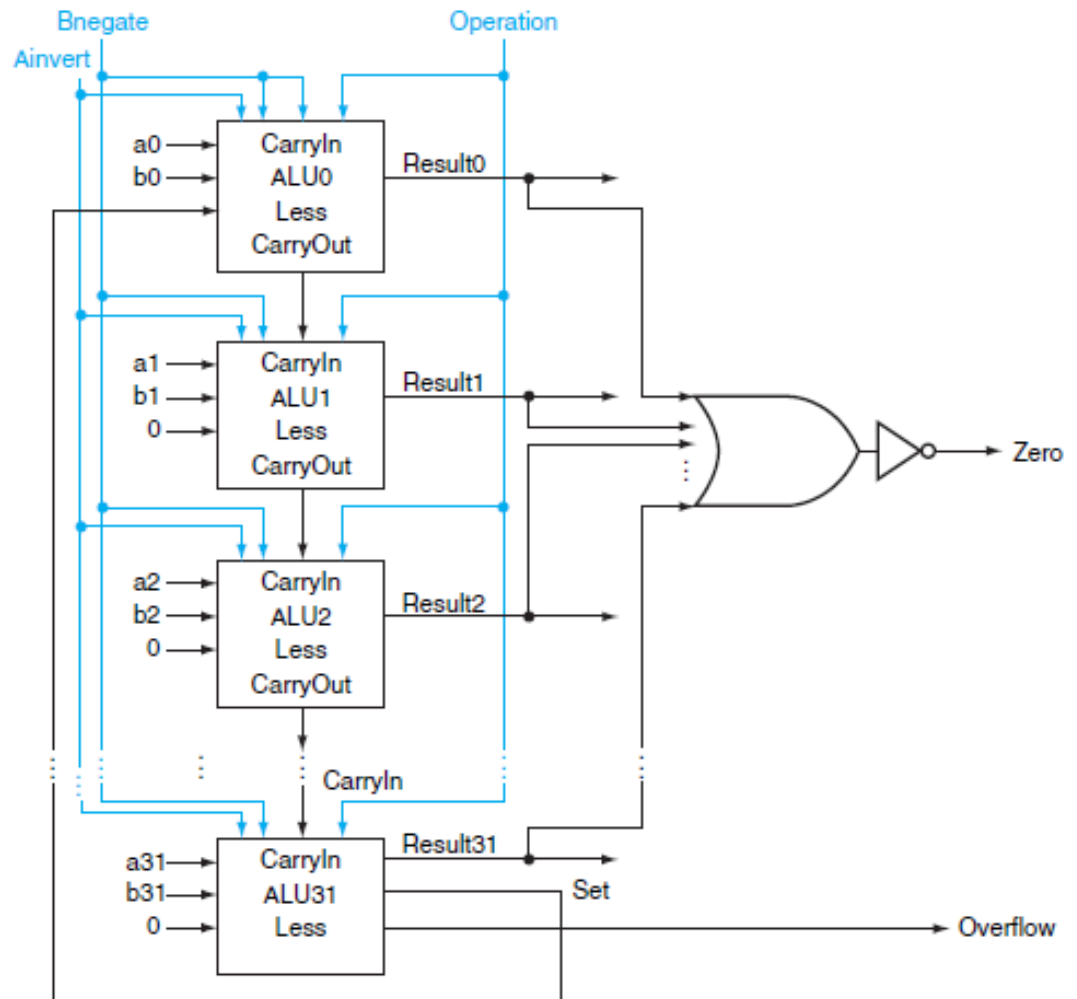
- Subtraction:
 - Both CarryIn and Binvert are 1
 - Combine into 1 signal “Bnegate”



A 32-Bit ALU

- Set on Less Than:

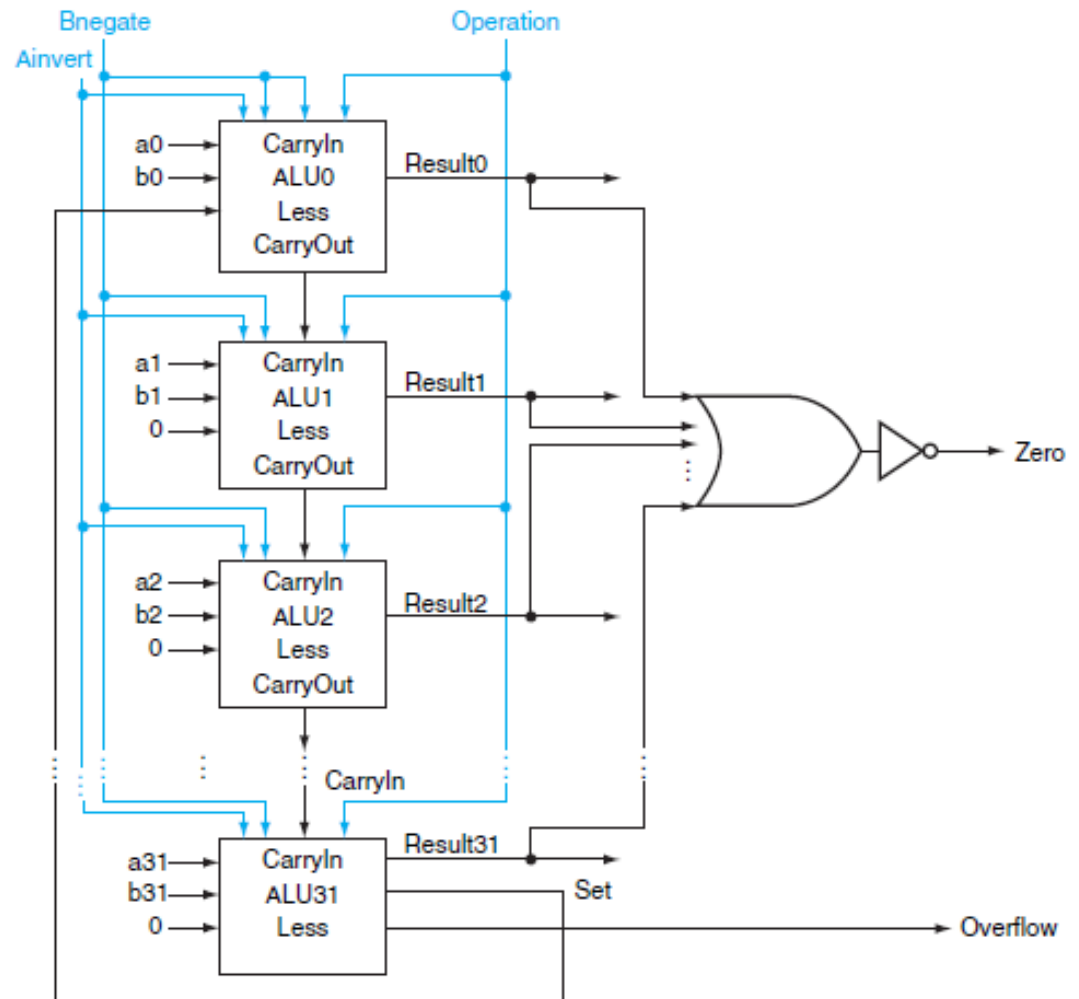- Less = 0
Bits 1-31
- Less = sign bit
Bit 0



A 32-Bit ALU

- Universal symbol for ALU

