


SEQUENTIAL LOGIC DESIGN

Introduction


- Combinational Circuits
 - Without memory
 - Outputs depend only on current inputs
 - Output determined after sufficient time has elapsed
- Sequential Circuits
 - Have memory
 - Outputs depend on inputs and previous outputs
 - Previous output stored even after waiting

Simple Sequential Circuits

 - Two inverters form a static memory cell
 - The previous output is stored by passing it back into the system
 - Will hold value as long as it has power applied



 - How to get a new value into the memory cell?
 - Selectively break feedback path
 - Load new value into cell



Sequential Circuits


- Latches
- Flip-flops
- Registers

Latches

- A latch is a memory element in which the output is equal to the value of the stored state inside the element and the state is changed whenever the appropriate inputs change.

Set-Reset Latch

 - Built from cross-coupled NOR gates
- Ability to force output to 0 (reset=1) or 1 (set=1)



State Machines

- A sequential circuit is described as a finite-state machine
 - A set of states
 - A function to determine the next state
 - A function to determine the output
 - Functions can still be represented by a truth table

Behavior of the S-R Latch

- States: {hold, set, reset, unstable}
- Next-State function:

S	R	State
0	0	hold
0	1	0
1	0	1
1	1	unstable

Behavior of the S-R Latch

- States: {hold, set, reset, unstable}
- Output function:


S	R	Q _{in}	Q _{out}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	?
1	1	1	?

Behavior of the S-R Latch

- State Diagram


- States: possible outputs
- Transitions: events that cause the system to change states (inputs)

 possible oscillation
between states 00 and 11




Behavior of the S-R Latch

 - Very difficult to observe R-S latch in the unstable state
 - One of R or S usually changes first
- Ambiguously returns to state 0-1 or 1-0
 - A so-called "race condition"
 - Or non-deterministic transition




Unclocked S-R Latch

 - In an unclocked circuit the outputs change whenever the inputs change.




Clocks

 - Clocks are regular periodic signals
 - Clock period is divided into two portions
 - When the clock is “high”, also called the duty cycle
 - When the clock is “low”
 - State changes occur on a clock edge
 - When the clock moves from low to high or from high to low




Edge-Triggered Methodology

 - Either the rising edge or the falling edge is active
 - Determined by implementation
 - Does not affect design
- Elements change on the active clock edge
 - All inputs sampled at the same time
 - All inputs must be valid (steady) at the active clock edge
- Clocked systems are also called synchronous systems.



Sequential Logic Design

 - Combinational logic elements are still used
- State elements provide valid inputs to the combinational logic block.
- Clock period must be long enough to allow all the signals in the combinational logic block to settle




Steady-State Abstraction

- All real circuits need time to update
 - The outputs do not change instantaneously after an input change
- A fundamental abstraction of digital design is to reason about steady-state behaviors
 - Look at outputs only after sufficient time has elapsed for the system to make its required changes and settle down
 - Memory of a system is represented as its state
 - Changes in system state are only allowed to occur at specific times


Clocked S-R Latch

 - In a clocked circuit, we control when the inputs are sampled.



Clocked S-R Latch

 - Controlling an R-S latch with a clock
 - Can't let R and S change while clock is active
 - Only have half of clock period for signal changes to propagate
 - Signals must be stable for the other half of clock period




Flip-Flops

- A flip-flop is a memory element for which the output is equal to the value of the stored state inside the element and for which the internal state is changed only on a clock edge.
 - Often built from clocked latches


D Flip-Flop

 - 2 Inputs
 - D, the data to be stored
 - C, the clock signal
- 2 Outputs
 - Q, the internal state
 - Q', the complement of Q



D Flip-Flop

 - When the clock is asserted, the flip-flop is “open”
 - If D is 1, the S-R latch is “set”
 - If D is 0, the S-R latch is “reset”
- When the clock is deasserted, the flip-flop is “closed”
 - The S-R latch is “holding”




D Flip-Flop

- Flip-Flops can be built to trigger on either the rising or falling clock edge
 - Remember this does not affect the design
- Flip-Flops can be built to trigger on the offset edge
 - If all Flip-Flops trigger on the positive edge, we can build one to trigger on the negative edge
 - We use cascading logic blocks


Cascading Logic Circuits

 - Connect output of one latch to input of another
- How to stop changes from racing through chain?
 - Need to control flow of data from one latch to the next
 - Advance from one latch per clock period
 - Must respect setup and hold time constraints to successfully capture input



Timing Methodologies

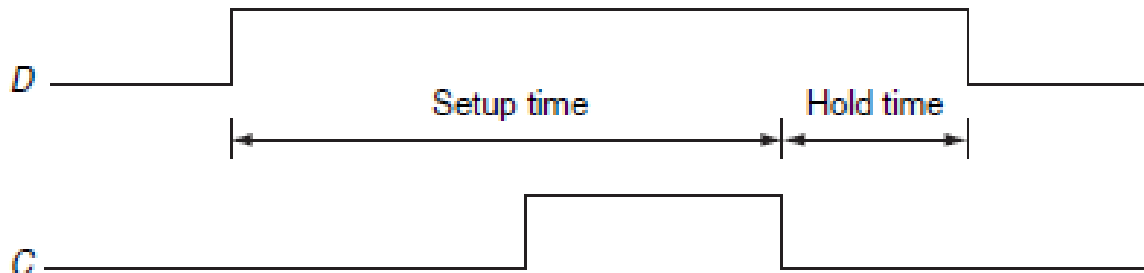- The set up time is the minimum time that the input must be valid before the clock edge.
- The hold time is the minimum time during which it must be valid after the clock edge.




Timing Methodologies

- Rules for interconnecting components and clocks
 - Guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for memory elements
 - Focus on systems with edge-triggered flip-flops
- Basic rules for correct timing:
 - (1) Correct inputs, with respect to time, are provided to the flip-flops
 - (2) No flip-flop changes state more than once per clocking event

Typical Timing Specifications

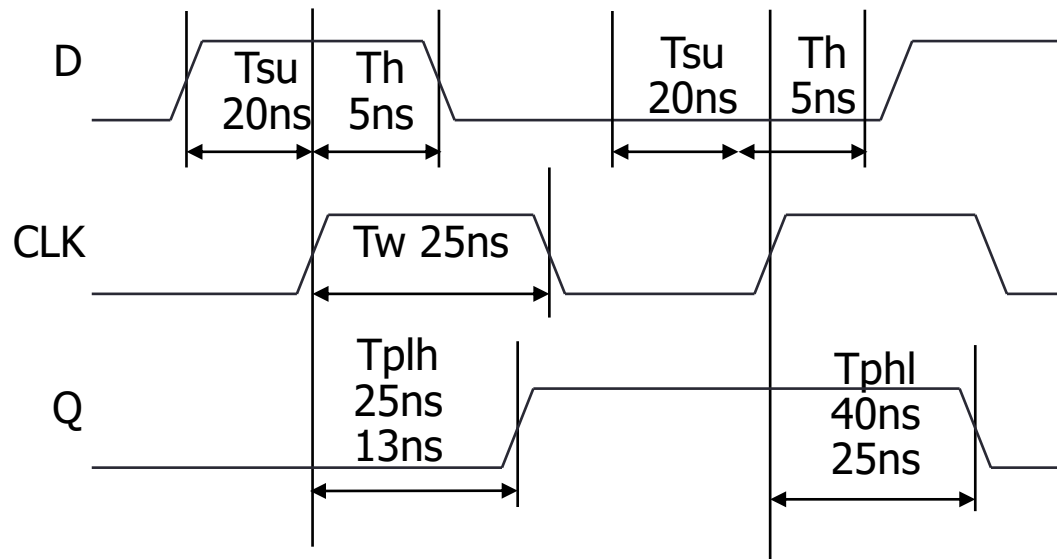
- Positive edge-triggered D flip-flop
 - Setup and hold times
 - Minimum clock width
 - Propagation delays (low to high, high to low, max and typical)



all measurements are made from the clocking event:
the rising edge of the clock

Cascading Edge-triggered Flip-Flops

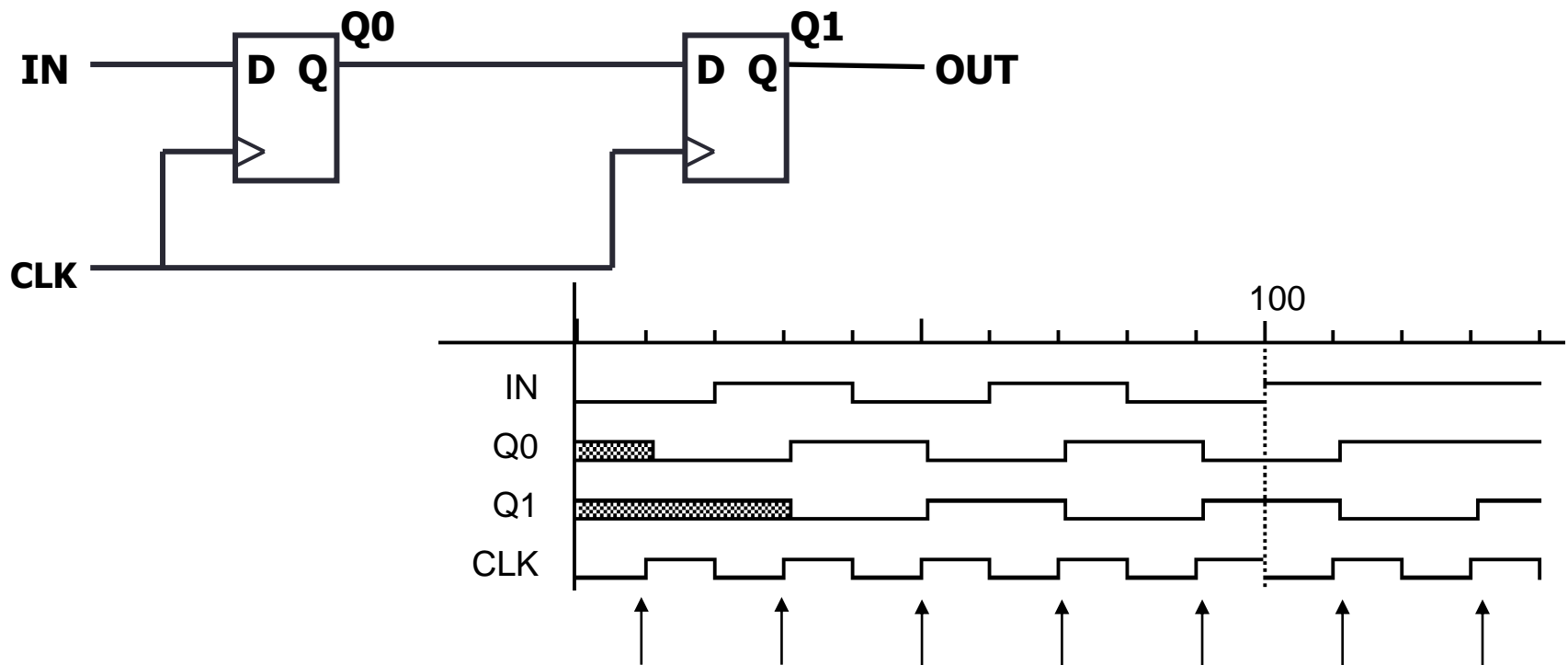- Consider setup/hold/propagation delays
 - prop must be $>$ hold




Clock Skew

- Correct behavior assumes next state of all storage elements determined by all storage elements at the same time
- This is difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic
- Clock skew is the difference in time between when two state elements see a clock edge

Clock Skew

 - If the clock skew is large enough, it may be possible for a state element to change and cause the input to another flip-flop to change before the clock edge is seen by the second flip-flop.
 - To avoid incorrect operation, we must increase the clock period to allow for the maximum clock skew.



original state: $IN = 0$, $Q0 = 1$, $Q1 = 1$


due to skew, next state becomes: $Q0 = 0$, $Q1 = 0$, and not $Q0 = 0$, $Q1 = 1$

Asynchronous Inputs

- Clocked synchronous circuits
 - Inputs, state, and outputs sampled or changed in relation to a common reference signal (called the clock)
- Asynchronous circuits
 - Inputs, state, and outputs sampled or changed independently of a common reference signal
 - Some system inputs must be asynchronous
 - reset signal, memory wait, user input
 - Unstable states are a major concern
- Asynchronous inputs to synchronous circuits
 - Because synchronous inputs are greatly preferred, we use a synchronizer


Synchronizer

 - Use a synchronizer to translate asynchronous input




Synchronizer

 - What happens if the asynchronous input is transitioning between 0 and 1?
 - The signal is not stable for the required setup and hold times
 - The synchronizer may enter a metastable state
 - The output will be neither 0 or 1
 - This situation is called synchronizer failure





Synchronization Failure

- Probability of failure can never be reduced to 0, but it can be reduced:
 - slow down the system clock: this gives the synchronizer more time to decay into a steady state; synchronizer failure becomes a big problem for very high speed systems
 - Narrow the “unknown” range of values: this makes for a very sharp "peak" upon which to balance
 - cascade two synchronizers: this effectively synchronizes twice (in subsequent clock cycles)

 

Handling Asynchronous Inputs

  - Never allow asynchronous inputs to fan-out to more than one flip-flop
 - Synchronize as soon as possible and then treat as synchronous signal




Sequential Hardware Elements

- Collections of flip-flops with similar controls and logic
 - Values in individual flip-flops are related
 - Shared clock signal
 - Similar logic at each stage
- Examples
 - Pattern Recognizer
 - Counter
 - Shift register
 - Data Register
 - Register File


Pattern Recognizer

 - Combinational function of input samples
 - In this case, recognizing the pattern 1001 on the single input signal




Counters

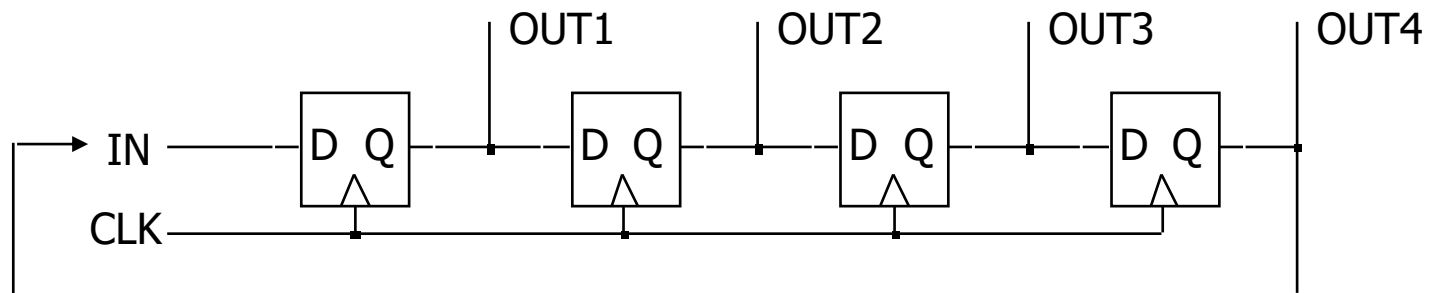- Sequences through a fixed set of patterns
 - In this case, 1000, 0100, 0010, 0001
 - If one of the patterns is its initial state (by loading or set/reset)




 - Mobius (or Johnson) counter
 - In this case, 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000




Shift Register

 - Holds samples of input
 - Store last 4 input values in sequence
 - 4-bit shift register:



Universal Shift Register

 - Holds 4 values
 - Serial or parallel inputs
 - Serial or parallel outputs
 - Permits shift left or right
 - Shift in new values from left or right




clear sets the register contents and output to 0

s1 and s0 determine the shift function

s0	s1	function
0	0	hold state
0	1	shift right
1	0	shift left
1	1	load new input


Design of Universal Shift Register

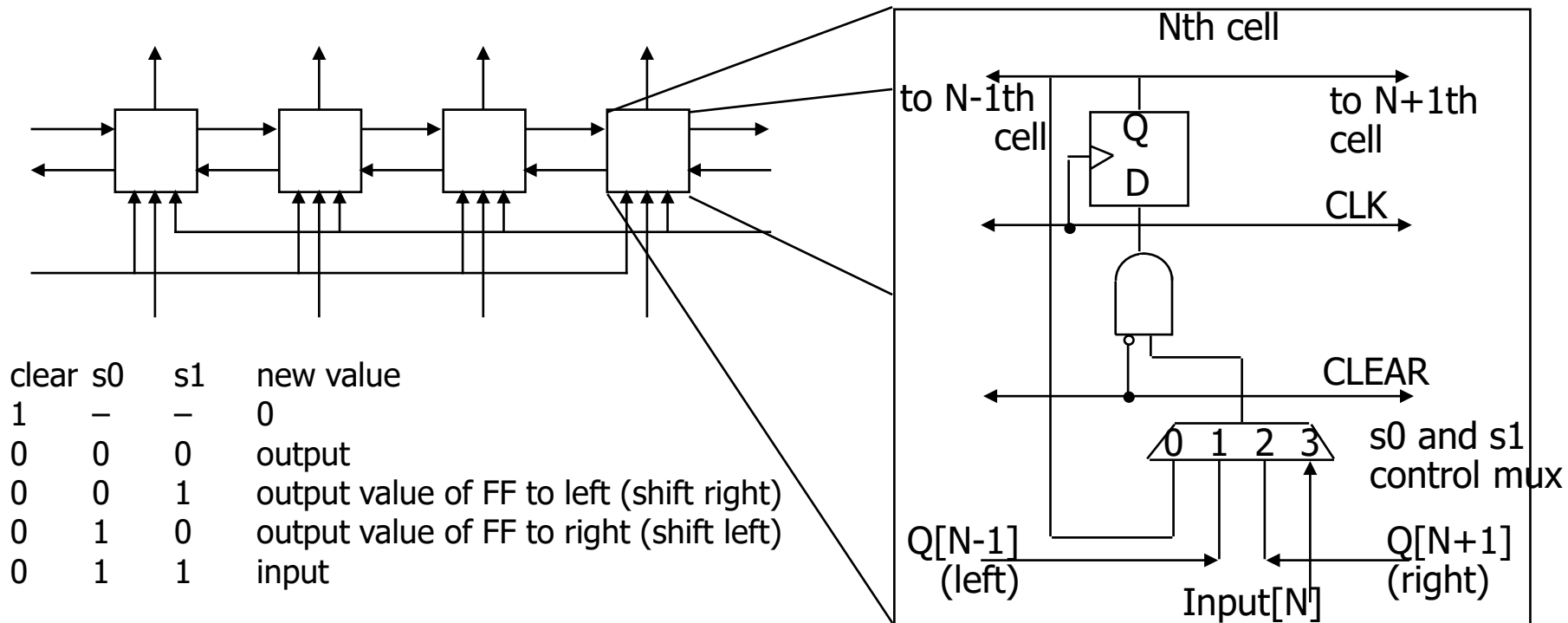- Consider one of the four flip-flops
 - New value at next clock cycle:



Data Register

 
- Capable of holding a single binary value
- Loads a new value when write is enabled
- 4-bit Data Register



Register Files

- A register file consists of a set of registers that can be read and written by supplying a register number to be accessed.

Register Files: Read

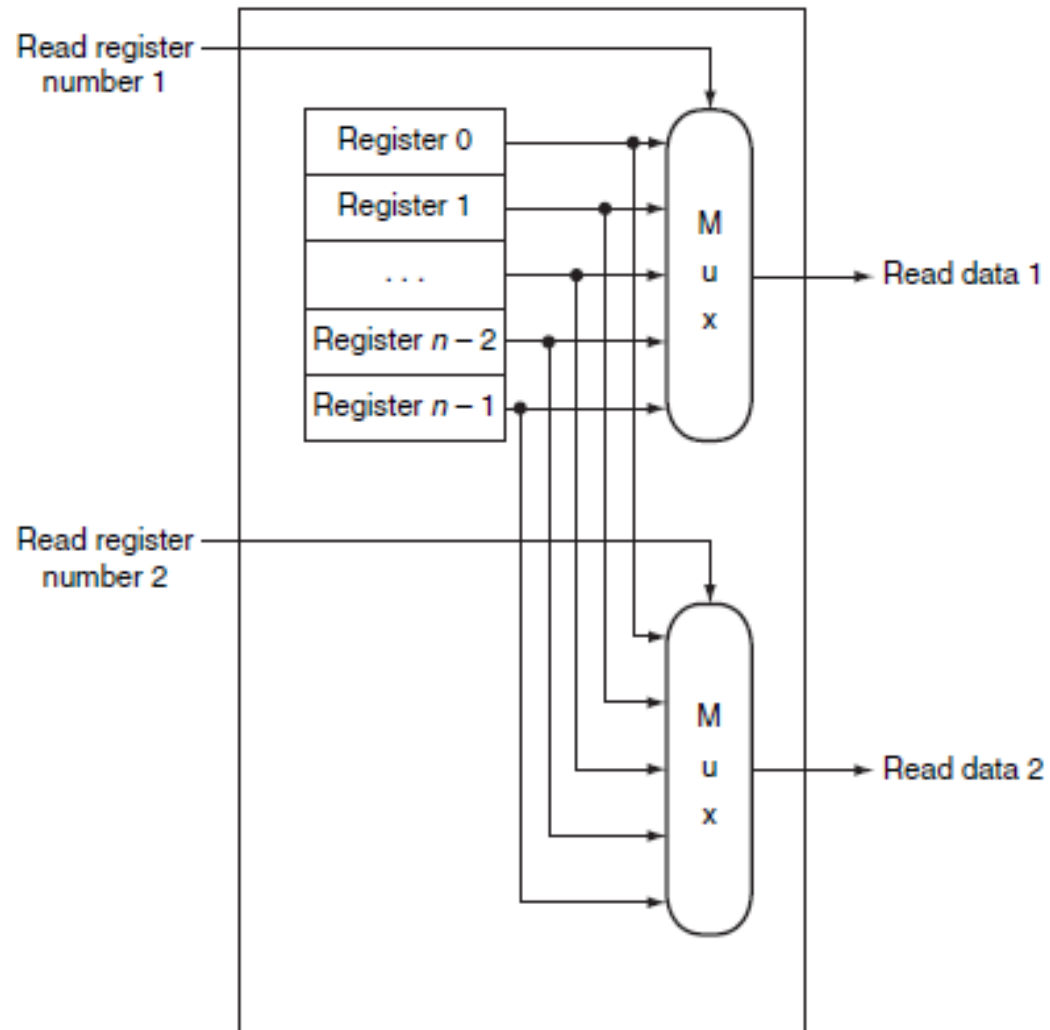

Register Files: Write

